

COIMBATORE INSTITUTE OF TECHNOLOGY
(Government Aided Autonomous Institution)
COIMBATORE 641 014**B.Tech. DEGREE EXAMINATIONS, SEPTEMBER 2022**
(Second Semester)**ARTIFICIAL INTELLIGENCE AND DATA SCIENCE BRANCH****21CS21 DIGITAL DESIGN**

Time : 3 Hours

Max: 75 marks

INSTRUCTIONS

1. Answer all questions in PART A and as per choice in PART B.
2. Part A and Part B questions should be answered separately in the same answer sheet.

PART:A**(10 X 2 = 20)**

- 1 Identify the value for the following equivalence: $(37.25)_{10} = (?)_6$
- 2 Consider $(123)_5 = (X8)_Y$. The number of possible solution(s) for X and Y is / are?
- 3 Let $f(x_1, x_2, \dots, x_n)$ be equal to 1 if and only if k or more of the variables are equal to 1 ($k \leq n$). How many prime implicants does this function have?
- 4 Express the following function $F(x, y, z) = xy + x'z$ to its canonical product-of-sum expression.
- 5 Find the max terms for the following : $F(P, Q, R) = (P + Q)(\sim P + \sim R)$ where $\sim X$ represents the complement of X.
- 6 Design a full Adder using only the universal NAND gates.
- 7 Outline the salient differences between latches and flip-flops.
- 8 Give the excitation table for S-R flip-flop. Outline the timing diagram for an S-R flip-flop with S and R values as '0110' and '1001' respectively.
- 9 Give a brief overview about EDO(Extended Data Out) RAM.
- 10 Illustrate the block diagram that shows L1 and L2 cache memories in a computer.

PART:B**(5 X 11 = 55)**

11. Design a 4-bit Binary-to-Gray code converter. Assume $B_4B_3B_2B_1$ represents 4-bit Binary number and $G_4G_3G_2G_1$ represents its 4-bit Gray code. **(6 + 5)**
 - a) Draw the truth table. Show K-map and derive the expression for G_i 's in terms of B_i 's.
 - b) Using the minimized expression, realize the logic circuit for the same.

(OR)

- 12 a.) Construct a Truth Table for a Headlight Warning System application which abides **(6 + 5)** with the following constraints:
 - Day driving does not require a head light.
 - Night driving requires a head light.
 The system accepts three parameters as inputs viz., H, I and D representing Headlight, Engine Ignition and Daytime respectively and yields an output W that represents a warning signal.
- b.) Given $(135)_x + (144)_x = (323)_x$. Find the base 'x' so that the preposition holds. Once the base 'x' is found, find the decimal equivalent of individual numbers given in the preposition.

Contd..

- 13 a) Draw the logic circuit of the parallel Adder, by realizing each full Adder using two half Adder circuits. (6 + 5)

- b) Minimize the following Boolean function by applying suitable algebraic laws.

$$F(A, B, C, D) = ABC'D' + ABC'D + AB'C'D + ABCD + AB'CD + ABCD' + AB'CD'$$

(OR)

- 14 Using Quine McClusky's method(QM method), simplify the below Boolean expression that possess don't care condition: (11)

$$F(A, B, C, D) = \sum_m (1, 5, 6, 12, 13, 14) + d(2, 4)$$

- 15 a) Outline the principles of a 2^n to n Encoder. Construct a Truth table for a 8:3 Encoder. Realize the logical circuit for the same. (6 + 5)
- b) With suitable illustration, brief about priority encoders.

(OR)

- 16 a) Devise a logical circuit such that it performs 4-Bit binary addition-cum-subtraction. (6 + 5)
- b) With a suitable illustration, explain about the philosophy behind Look-Ahead Carry Adder?

- 17 Give the block diagram for a primitive J-K Flip-flop along with its excitation table. Give the timing diagram for a positive edge-triggered J-K flip-flop for the following sequence: J = '00110011' and K = '11001001' (6 + 5)

(OR)

- 18 a) Design an asynchronous Mod-6 up counter using J-K flip-flop. (6 + 5)
- b) What are bidirectional shift registers? Show how bidirectional shifts are achieved by considering a 4-bit bidirectional shift register.

- 19 a) Describe about the various types of read-only memories. (6 + 5)
- b) Give short notes on Flash memories. Give a comparative study between flash memory and ROM.

(OR)

- 20 Show a basic 16X8-bit ROM array programmed for a 4-bit Binary -to-Gray conversion (6 + 5)
